


GTU
DEPARTMENT OF
COMPUTER ENGINEERING

CSE 331 – Autumn 2022


HOMEWORK 2
REPORT

SÜLEYMAN GÖLBOL
1801042656


Main Components

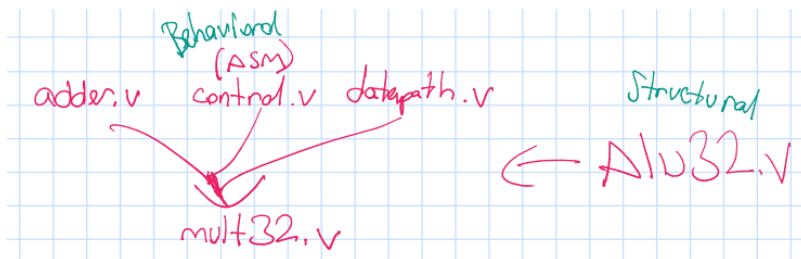

Multiplication Component

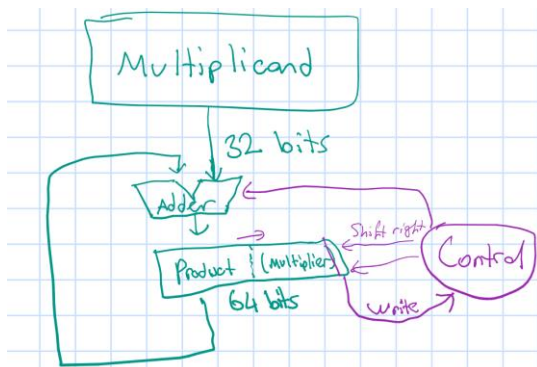

HL STATE MACHINE

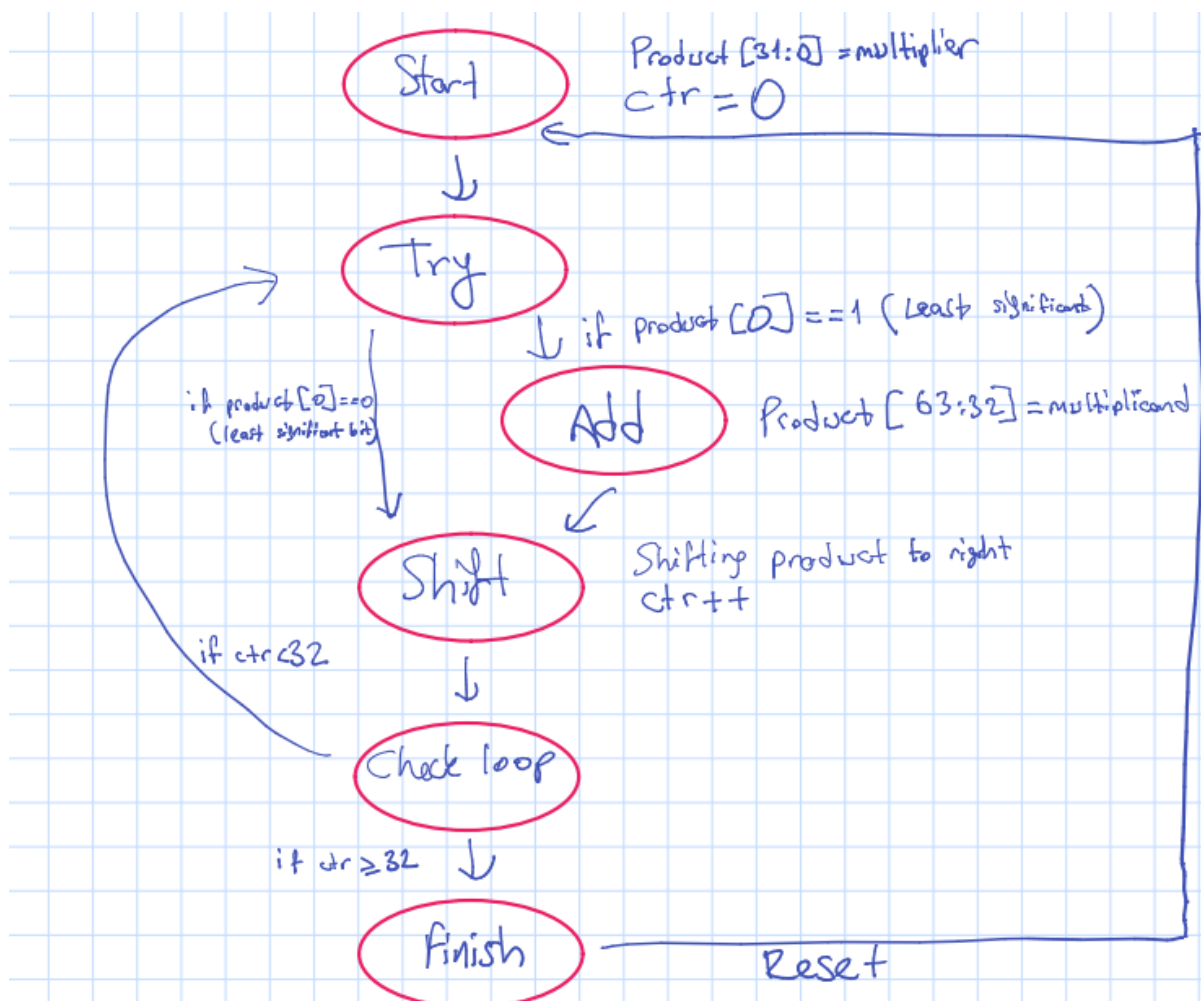

FINITE STATE MACHINE OF VARIABLES

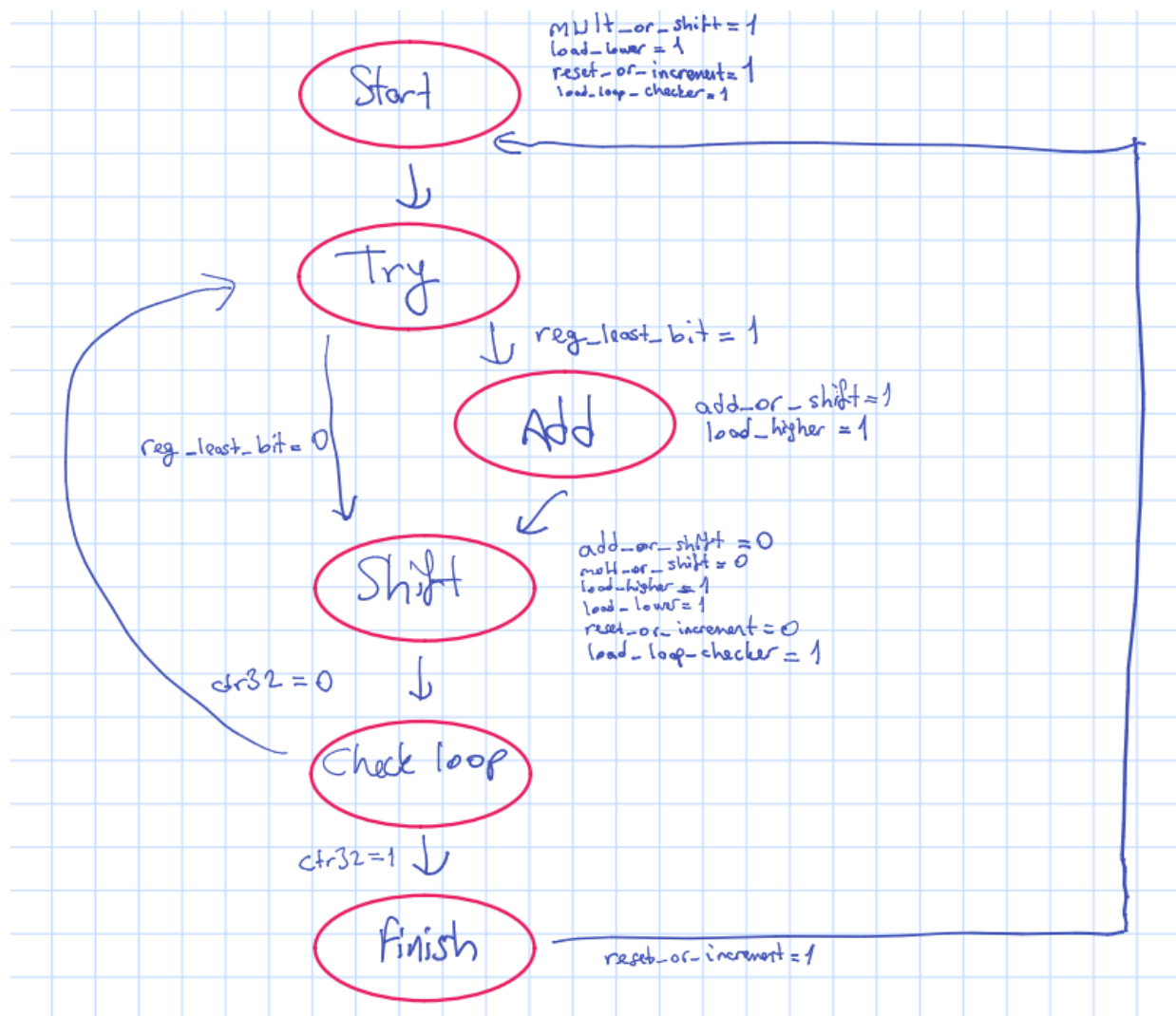


TABLE FOR EVERY STATE

States	R[2]	R[1]	R[0]	input	Next	N[2]	N[1]	N[0]
Start	0	0	0	1	Try	0	0	1
Try	0	0	1	reg_least_bit	Add	0	1	0
Try	0	0	1	$\neg reg_least_bit$	Shift	0	1	1
Add	0	1	0	1	Shift	0	1	1
Shift	0	1	1	1	check loop	1	0	0
check loop	1	0	0	$\neg ctr32$	try	0	0	1
check loop	1	0	0	$ctr32$	finish	1	0	1
finish	1	0	1	reset	Start	0	0	0
finish	1	0	1	$\neg reset$	finish	1	0	1

DERIVING LOGIC

$$N2 = R2'.R1.R0 + R2.R1'.R0' + \text{ctr32} + R2.R1'.R0.\text{reset}'$$

$$N1 = R2'.R1'.R0 + R2'.R1.R0'$$

$$N0 = R2'.R1'.R0' + R2'.R1'.R0.\text{reg_least_bit}$$

$$+ R2'.R1.R0' + R2.R1'.R0' + R2.R1'.R0.\text{reset}$$

$$\text{mult_or_shift} = R2'.R1'.R0'$$

$$\text{load_lower} = R2'.R1'.R0' + R2'.R1.R0$$

$$\text{load_loop_checker} = R2'.R1'.R0' + R2'.R1.R0$$


$$\text{reset_or_increment} = R2'.R1'.R0'$$

$$\text{add_or_shift} = R2'.R1.R0'$$







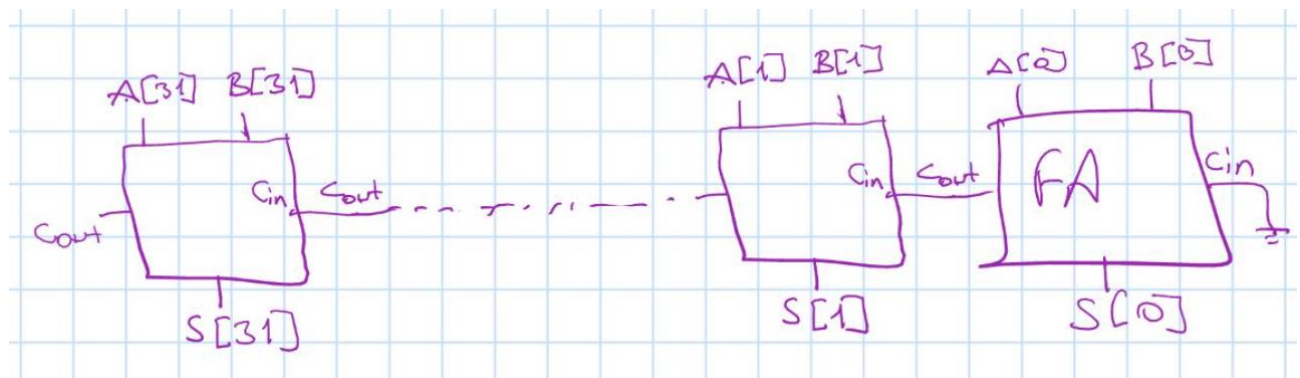


$$\text{load_higher} = R2'.R1.R0' + R2.R1.R0$$

1. ADDER COMPONENT


For adder component, I created a 1-bit full adder. To create 32 bits adder, I used every full adder's "carry out" value to connect. Then I put the output into 32 bits sum variable.




Testing

Wave - Default		Msgs
		
	 /testbench_adder/a	000000000000000000001011101110110010
	 /testbench_adder/c...	0
	 /testbench_adder/b	0000000000000000000010101101100111
	 /testbench_adder/s...	000000000000000000001110011100011001
	 /testbench_adder/c...	HiZ

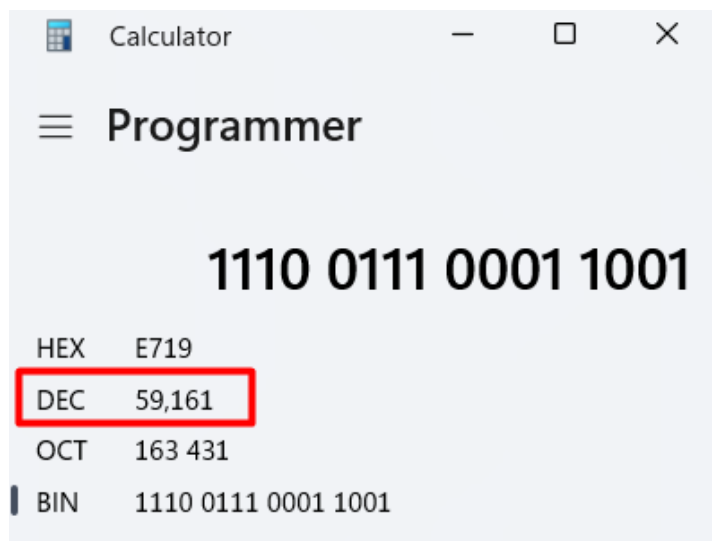I tried to add 48050 and 11111. The sum should be 59161.




2. CONTROL COMPONENT

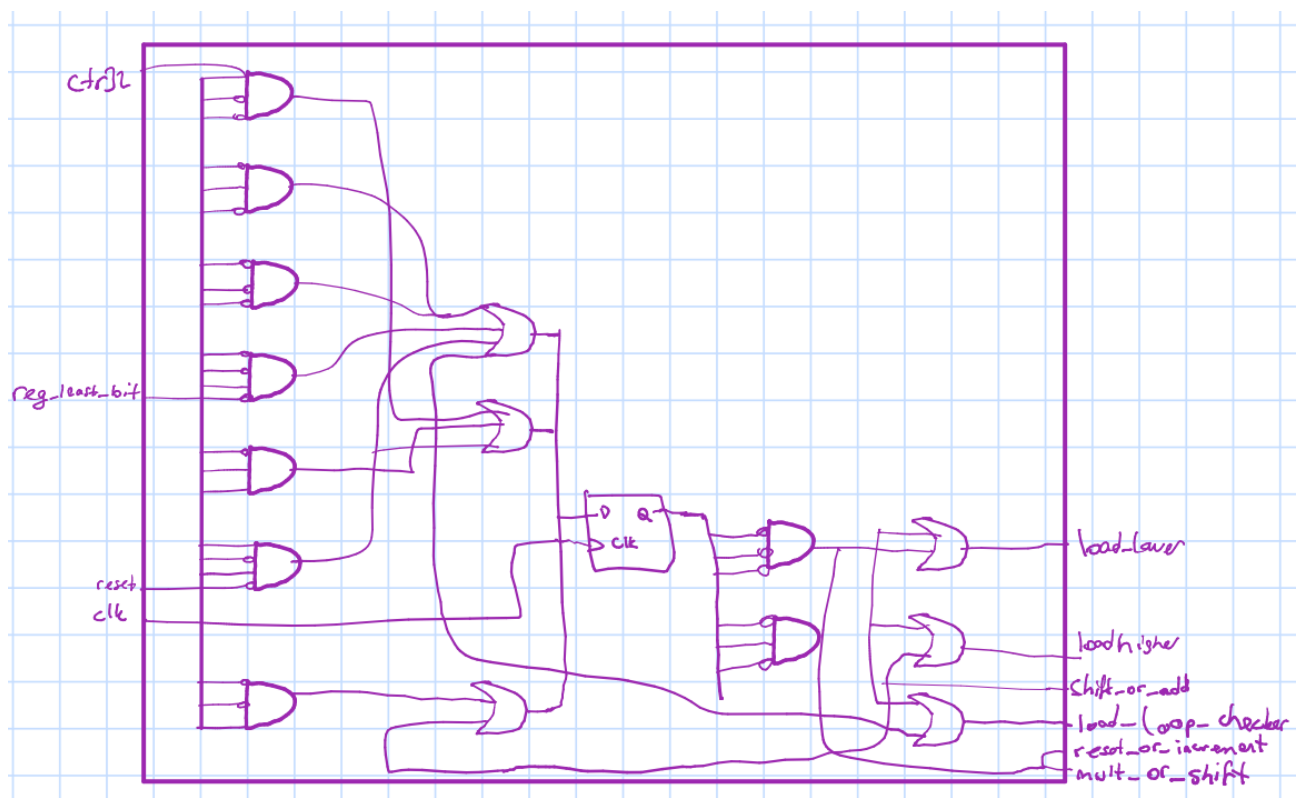


For the control part, I needed to use state table variables values to achieve mult_or_shift, reset_or_increment, load_loop_checker, load_higher, load_lower values using inputs reset, clk and reg_least_bit.

At the end values are like that.

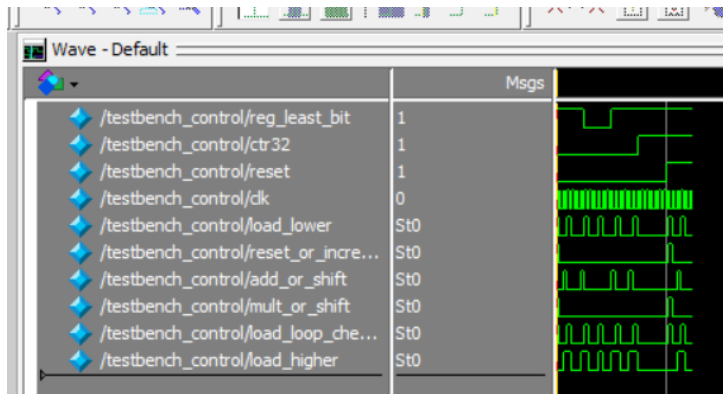

3. DATAPATH COMPONENT

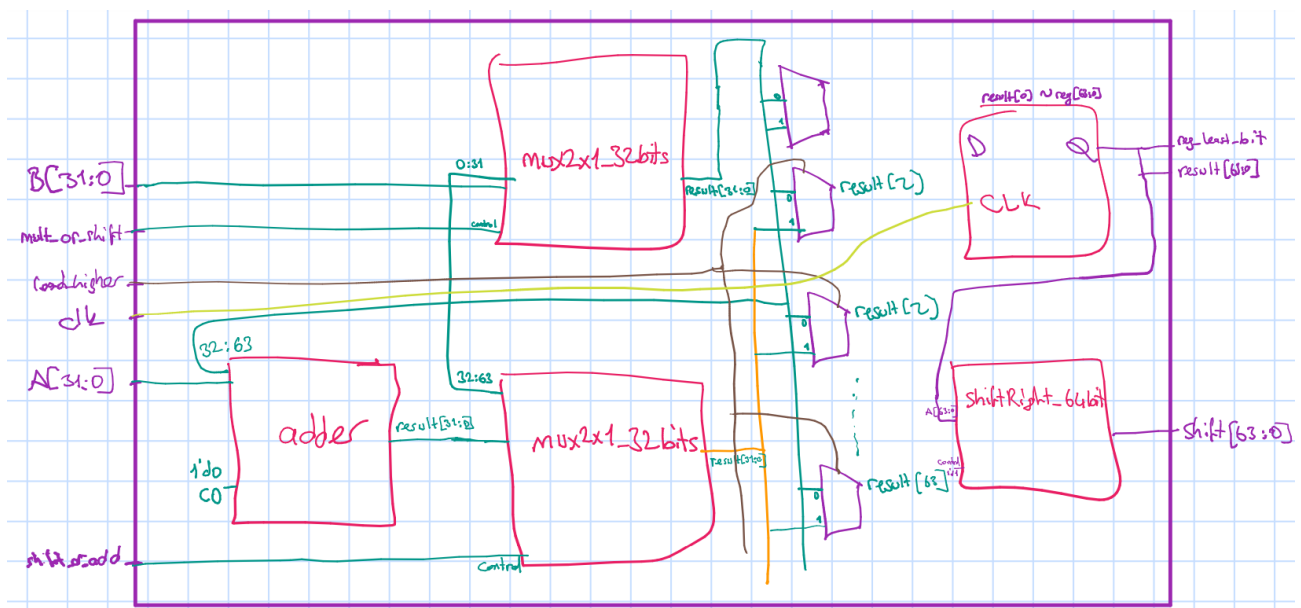

For the datapath component I used 2 multiplexer to select current state or selecting 64 bit number to produce. Multiplexer above takes first 32 bits and below takes last 32 bits. Mult_or_Shift is connected to first multiplexer to control selection. Below, add_or_shift is connected to multiplexer to control selection. Shiftright_64bit has control signal which is 1, so it will shift right the 64 bit number.

Since it will continue until 32 there is a loop checker and ctr32 connected to incrementer. Incrementer uses mux2x1_8bits, adder_8bits and setonlessthan_32bits to increment the number.

Also, to prevent repetition for array-like variables, I used generate keyword with “genvar” variable.

```
// generation variable to prevent repetition
genvar i;
// NOTE: FOR LOOP IN GENERATE IS NOT BEHAVIORAL. IT JUST TO PREVENT REPETITION.
// for loop for and1
generate
    for (i=0; i<=62; i = i+1) begin: mymux
        mux2x1_lbit mux(A[i], A[i+1], control, result[i]);
    end
endgenerate
```

It's just a helper not to write same thing tens of times.

4. MULT32.V


Multiplier module connects them all to multiply number.

```
control mycontroller (reg_least_bit, ctr32, reset, clk, add_or_shift, load_higher, mult_or_shift,
load_lower, reset_or_increment, load_loop_checker);
datapath mydatapath (add_or_shift, load_higher, mult_or_shift, load_lower, reset_or_increment, load_loop_checker,
a, b, clk, shift_wire, result, reg_least_bit, ctr32);
```

As it seen first uses control then uses datapath module with all needed parameters.

Testing

Multiplying $67 * 883$

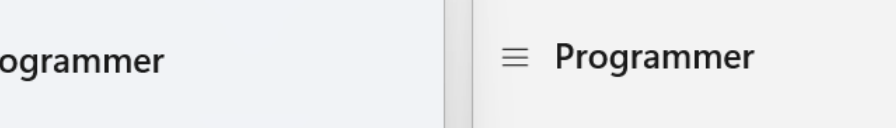


The image displays two side-by-side screenshots of the Windows Calculator application in Programmer mode. Both windows have the title bar 'Calculator' and standard window controls. The left window shows the display '0100 0011' and a list of conversion options: HEX 43, DEC 67, OCT 103, and BIN 0100 0011. The 'DEC 67' option is highlighted with a red rectangular box. The right window shows the display '0011 0111 0011' and a list of conversion options: HEX 373, DEC 883, OCT 1 563, and BIN 0011 0111 0011. The 'DEC 883' option is highlighted with a red rectangular box.

After adding waves in ModelSim app to testbench, this is the result.

[illegible]

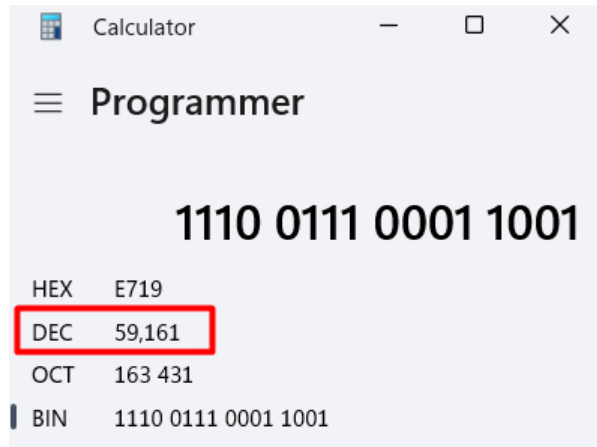This is the result as expected because $67 * 883 = 59161$



5. ALU32.V

Alu32 module have a multiplexer to select one of the 8 options.

000->ADD	100->AND
001->SUB	101->OR
010->MULT	110->SLT
011->XOR	111->NOR


```

adder gatea (a,b, 1'b0, add_wire);
xor_32bits gateb (a, b, xor_wire);
substractor_32bits gatec (a, b, subs_wire);
mult32 gated(a, b, reset, clk, mult_wire);
slt_32bits gatee (a, b, slt_wire);
nor_32bits gatef (a,b, nor_wire);
and_32bits gateg (a,b, and_wire);
or_32bits gateh (a,b, or_wire);
mux8x1_64bits gatei({32'd0,add_wire}, {32'd0,subs_wire}, mult_wire, {32'd0,xor_wire},
                    {32'd0,and_wire}, {32'd0,or_wire}, {32'd0,slt_wire}, {32'd0,nor_wire}, ALUop, result);

```


Adder

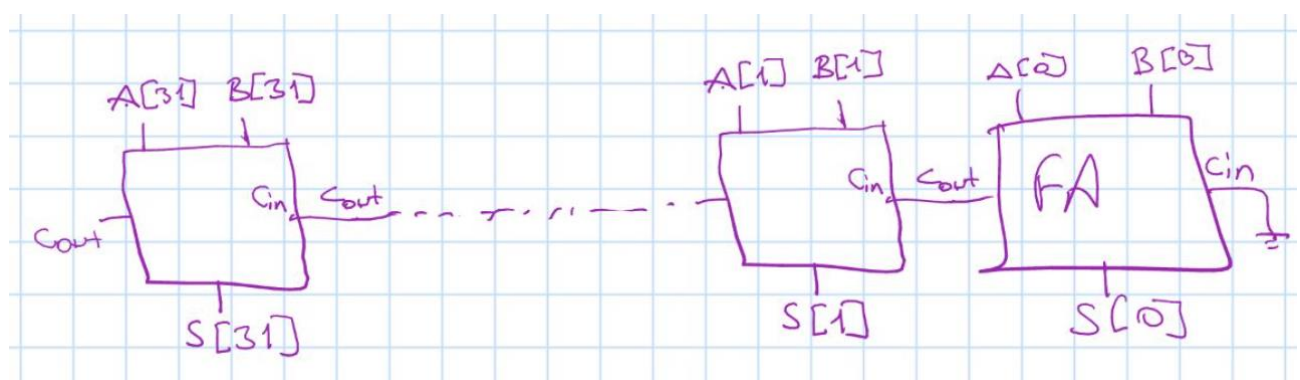Like I wrote above, it's made by connecting full adders.



A and B Inputs are: 12345 and 21543. $A+B = 33888$

```
# ALUOp: 000
# A and B:
# 000000000000000000011000000111001
# 0000000000000000000101010000100111
# result:
# 000000000000000001000010001100000
```

 Programmer

12345 + 21543 =
33,888

HEX	8460
DEC	33,888
OCT	102 140
BIN	1000 0100 0110 0000

Sub

```
module substractor_32bits(input [31:0] a, input [31:0] b, output [31:0] result);
    wire [31:0] wirevar;


    xor_32bits gate1(b, 32'b11111111111111111111111111111111, wirevar);
    adder gate2(a, wirevar /*b*/, 1'b1, result);

endmodule
```

It only takes 2's complement for sub



```
ALUOp: 001
A and B:
000000000000000000011000000111001
0000000000000000000101010000100111
result:
1111111111111111111101110000010010
```

A and B Inputs are: 12345 and 21543. $A-B = -9198$

 Programmer

1111 1111 1111 1111 1101 1100 0001 0010


HEX	FFFF DC12
DEC	-9,198
OCT	37 777 756 022
BIN	1111 1111 1111 1111 1101 1100 0001 0010

 DWORD MS Mv

Mult

```
ALUop: 010
A and B:
00000000000000000011000000111001
000000000000000000101010000100111
result:
00001111110110100000110010101111
```

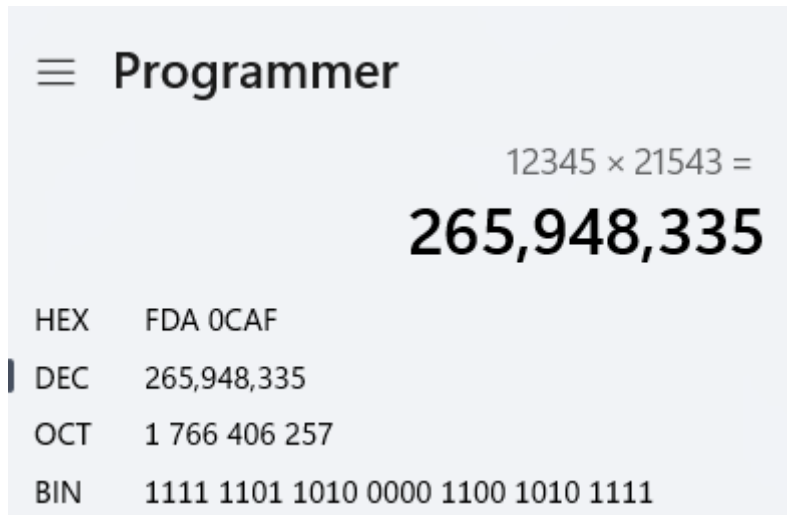A and B Inputs are: 12345 and 21543. $A*B= 265948335$




Ignore 0's in the beginning in the mult result.

Important Note:

ModelSim is printing all intermediate stages for multiplication. Please ignore Other AluOp:010 results and look only to the last 'ALUop:010' result.

Xor

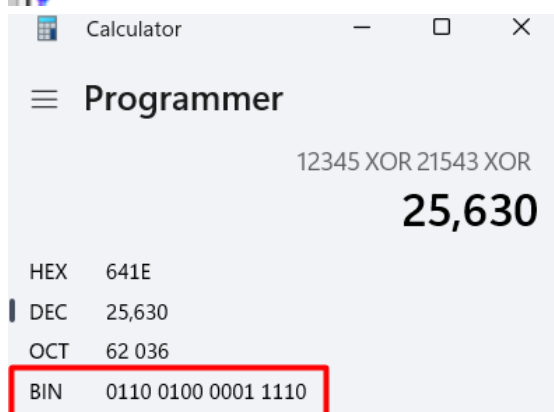
```
# ALUop: 011
# A and B:
# 00000000000000000011000000111001
# 000000000000000000101010000100111
# result:
# 000000000000000000110010000011110
#
```



A and B Inputs are: 12345 and 21543. Result is same.

And
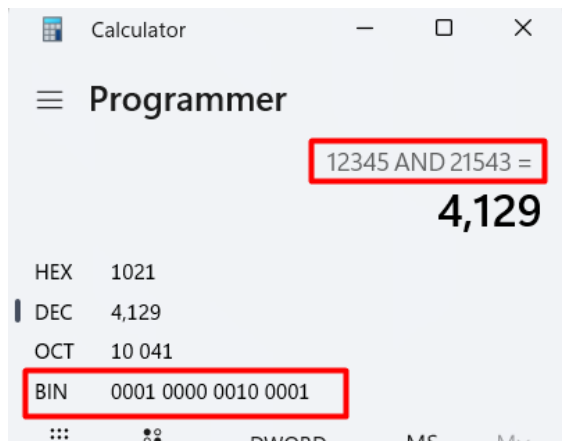
```
# ALUop: 100
# A and B:
# 0000000000000000000011000000111001
# 00000000000000000000101010000100111
# result:
# 000000000000000000001000000100001
```



Or

```
# ALUop: 101
# A and B:
# 0000000000000000000011000000111001
# 00000000000000000000101010000100111
# result:
# 00000000000000000000111010000111111
```



They are same.

Slt

```
1 module slt_32bits (input [31:0] A, input [31:0] B, output [31:0] result);
2
3 wire [31:0] wirevar;
4
5 // generation variable to prevent repetition
6 genvar i;
7 // for loop for andl
8 generate
9     for (i=1; i<32; i = i+1) begin: mynotgate
10         not notgate(result[i], 1'b1);
11     end
12 endgenerate
13
14 subtractor_32bits gatel(A, B, wirevar);
15 or (result[0], wirevar[31], 1'b0);
16
17 endmodule
```

First 32 bits are full of 0's. And the last bit is found out by using subtractions most significant bit.

```
# ALUop: 110
# A and B:
# 0000000000000000000011000000111001
# 00000000000000000000101010000100111
# result:
# 000000000000000000000000000000001
#
```

Since A(12345) is smaller than B(21543), result will be 1.

Nor

Just nors every bit.

```
# A and B:
# 0000000000000000000011000000111001
# 00000000000000000000101010000100111
# result:
# 11111111111111111000101111000000
#
```

≡ Programmer

12345 NOR 21543 =
~~-29,760~~

HEX FFFF 8BC0

DEC -29,760

OCT 37 777 705 700

BIN 1111 1111 1111 1111 1000 1011 1100 0000

Results are same.