

CSE331 – Computer Arithmetic 1

Unsigned Binary Integers

- ▶ Unsigned binary numbers are typically used to represent computer addresses or other values that are guaranteed not to be negative.
- ▶ An n-bit unsigned binary integer $A = a_{n-1} a_{n-2} \dots a_1 a_0$ has a value of

$$\sum_{i=0}^{n-1} a_i \cdot 2^i$$

- ▶ What is 1011 as an unsigned integer?
- ▶ An n-bit unsigned binary integer has a range from 0 to $2^n - 1$.
- ▶ What is the value of the 8-bit unsigned integer 10000001?

Signed Binary Integers

- ▶ Signed binary numbers are typically used to represent data that is either positive or negative.
- ▶ The most common representation for signed binary integers is the two's complement format.
- ▶ An n-bit 2's comp. binary integer $A = a_{n-1} a_{n-2} \dots a_1 a_0$ has a value of

$$-a_{n-1} \cdot 2^{n-1} + \sum_{i=0}^{n-2} a_i \cdot 2^i$$

- ▶ What is 1011 as a 2's comp. integer?
- ▶ An n-bit 2's comp. binary integer has a range from -2^{n-1} to $2^{n-1} - 1$.
- ▶ What is the value of the 2's comp. Integer 10000001?

Two's Complement Negation

- ▶ To negate a two's complement integer, invert all the bits and add a one to the least significant bit.

- ▶ What are the two's complements of

$$\begin{array}{r} 6 = 0110 \longrightarrow 1001 \\ \quad \quad \quad + \quad 1 \\ \hline \quad \quad 1010 = -6 \end{array}$$

$$\begin{array}{r} -4 = 1100 \longrightarrow 0011 \\ \quad \quad \quad + \quad 1 \\ \hline \quad \quad 0100 = 4 \end{array}$$

- ▶ What is the value of the two's complement integer 1111 1111 1111 1101 in decimal?
- ▶ What is the value of the unsigned integer 1111 1111 1111 1101 in decimal?

Two's Complement Addition

- ▶ To add two's complement numbers, add the corresponding bits of both numbers with carry between bits.

- ▶ For example,

$3 = 0011$	$-3 = 1101$	$-3 = 1101$	$3 = 0011$
$+ 2 = 0010$	$+ -2 = 1110$	$+ 2 = 0010$	$+ -2 = 1110$
<hr/>	<hr/>	<hr/>	<hr/>
$5 = 0101$	$-5 = 1011$	$-1 = 1111$	$1 = 0001$

- ▶ Unsigned and two's complement addition are performed exactly the same way, but how they detect overflow differs.

Two's Complement Subtraction

- ▶ To subtract two's complement numbers we first negate the second number and then add the corresponding bits of both numbers.
- ▶ For example:

$$\begin{array}{r} 3 = 0011 \\ - 2 = 0010 \\ \hline \end{array}$$



$$\begin{array}{r} 3 = 0011 \\ + -2 = 1110 \\ \hline 1 = 0001 \end{array}$$

Overflow

- ▶ When adding or subtracting numbers, the sum or difference can go beyond the range of representable numbers.

- ▶ This is known as overflow. For example, for two's complement numbers,

$5 = 0101$	$-5 = 1011$	$5 = 0101$	$-5 = 1011$
$+ 6 = 0110$	$+ -6 = 1010$	$- -6 = 1010$	$- +6 = 0110$
-----	-----	-----	-----
$-5 = 1011$	$5 = 0101$	$-5 = 1011$	$5 = 0101$

- ▶ Overflow creates an incorrect result that should be detected.

2's Comp – Detecting Overflow

- ▶ When adding two's complement numbers, overflow will only occur if
 - the numbers being added have the same sign
 - the sign of the result is different

- ▶ If we perform the addition

$$\begin{array}{r} a_{n-1} \ a_{n-2} \ \dots \ a_1 \ a_0 \\ + \ b_{n-1} \ b_{n-2} \ \dots \ b_1 \ b_0 \\ \hline = s_{n-1} \ s_{n-2} \ \dots \ s_1 \ s_0 \end{array}$$

- ▶ Overflow can be detected as $V = a_{n-1} \cdot b_{n-1} \cdot \overline{s_{n-1}} + \overline{a_{n-1}} \cdot \overline{b_{n-1}} \cdot s_{n-1}$

- ▶ Overflow can also be detected as

$V = c_n \otimes c_{n-1}$, where c_{n-1} and c_n are the carry in and carry out of the most significant bit.

Unsigned – Detecting Overflow

- ▶ For unsigned numbers, overflow occurs if there is carry out of the most significant bit.

$$V = c_n$$

- ▶ For example,

$$\begin{array}{r} 1001 = 9 \\ + 1000 = 8 \\ \hline 0001 = 1 \end{array}$$

- ▶ With the MIPS architecture
 - Overflow exceptions occur for two's complement arithmetic
 - add, sub, addi
 - Overflow exceptions do not occur for unsigned arithmetic
 - addu, subu, addiu

Shift Operations

- ▶ The MIPS architecture defines various shift operations:
 - (a) `sll r1, r2, 3` `r2 = 10101100` (shift left logical)
 `r1 = 01100000`
 - shift in zeros to the least significant bits
 - (b) `srl r1, r2, 3` `r2 = 10101100` (shift right logical)
 `r1 = 00010101`
 - shift in zeros to the most significant bits
 - (c) `sra r1, r2, 3` `r2 = 10101100` (shift right arithmetic)
 `r1 = 11110101`
 - copy the sign bit to the most significant bits
- ▶ There are also versions of these instructions that take three register operands.

Logical Operations

- ▶ In the MIPS architecture logical operations (and, or, xor) correspond to bit-wise operations.

(a) and r1, r2, r3 r3 = 1010 (r1 is 1 if r2 and r3 are both one)
 r2 = 0110
 r1 = 0010


(b) or r1, r2, r3 r3 = 1010 (r1 is 1 if r2 or r3 is one)
 r2 = 0110
 r1 = 1110

(c) xor r1, r2, r3 r3 = 1010 (r1 is 1 if r2 and r3 are different)
 r2 = 0110
 r1 = 1100

- ▶ Immediate versions of these instructions are also supported.

ALU Interface

 - ▶ We will be designing a 32-bit ALU with the following interface.



Z = 1, if Result = 0

V = 1, if Overflow

C₃₂ = 1, if Carry-Out

ALUOp	Function
000	AND
001	OR
010	ADD
110	SUBTRACT
111	SET-ON-LESS-THAN

Set-on-less-than

- ▶ The set-on-less instruction
 slt \$s1, \$s2, \$s3
 sets \$s1 to '1' if ($\$s2 < \$s3$) and to '0' otherwise.
- ▶ This can be accomplished by
 - subtracting \$s3 from \$s2
 - setting the least significant bit to the sign bit of the result
 - setting all other bits to zero
 - if overflow occurs the sign bit needs to be inverted

- ▶ For example,


$$\begin{array}{r} \$s2 = 1010 \\ -\$s3 = 1011 \\ \hline = 1111 \\ \$s1 = 0001 \end{array}$$

$$\begin{array}{r} \$s2 = 0111 \\ -\$s3 = 0100 \\ \hline = 0011 \\ \$s1 = 0000 \end{array}$$

Full Adder

- ▶ A fundamental building block in the ALU is a full adder (FA).
- ▶ A FA performs a one bit addition.

$$a_i + b_i + c_i = 2c_{i+1} + s_i$$

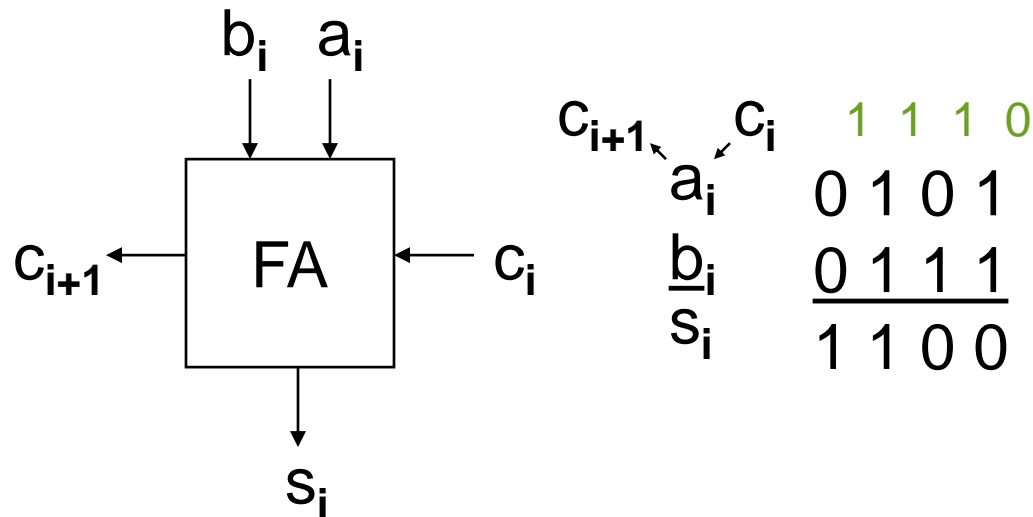

Full Adder Logic Equations

- ▶ s_i is '1' if an odd number of inputs are '1'.
- ▶ c_{i+1} is '1' if two or more inputs are '1'.

a_i	b_i	c_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$s_i = \bar{a}_i \bar{b}_i c_i + \bar{a}_i b_i \bar{c}_i + a_i \bar{b}_i \bar{c}_i + a_i b_i c_i$$

$$s_i = a_i \otimes b_i \otimes c_i$$

$$c_{i+1} = \bar{a}_i b_i c_i + a_i \bar{b}_i c_i + a_i b_i \bar{c}_i + a_i b_i c_i$$

$$c_{i+1} = a_i b_i + a_i c_i + b_i c_i$$

$$c_{i+1} = a_i b_i + c_i(a_i + b_i)$$

$$c_{i+1} = a_i b_i + c_i(a_i \otimes b_i)$$


Full Adder Design

- ▶ One possible implementation of a full adder uses nine gates.

$$s_i = a_i \oplus b_i \oplus c_i$$


$$c_{i+1} = a_i b_i + c_i(a_i \oplus b_i)$$
 
$$a_i \oplus b_i = (a_i + b_i) \overline{a_i b_i}$$




1-Bit ALU

 - ▶ The full adder, an xor gate, and a 4-to-1 mux are combined to form a 1-bit ALU.



ALUOp	Function
000	AND
001	OR
010	ADD
110	SUBTRACT
111	SET-ON-LESS-THAN

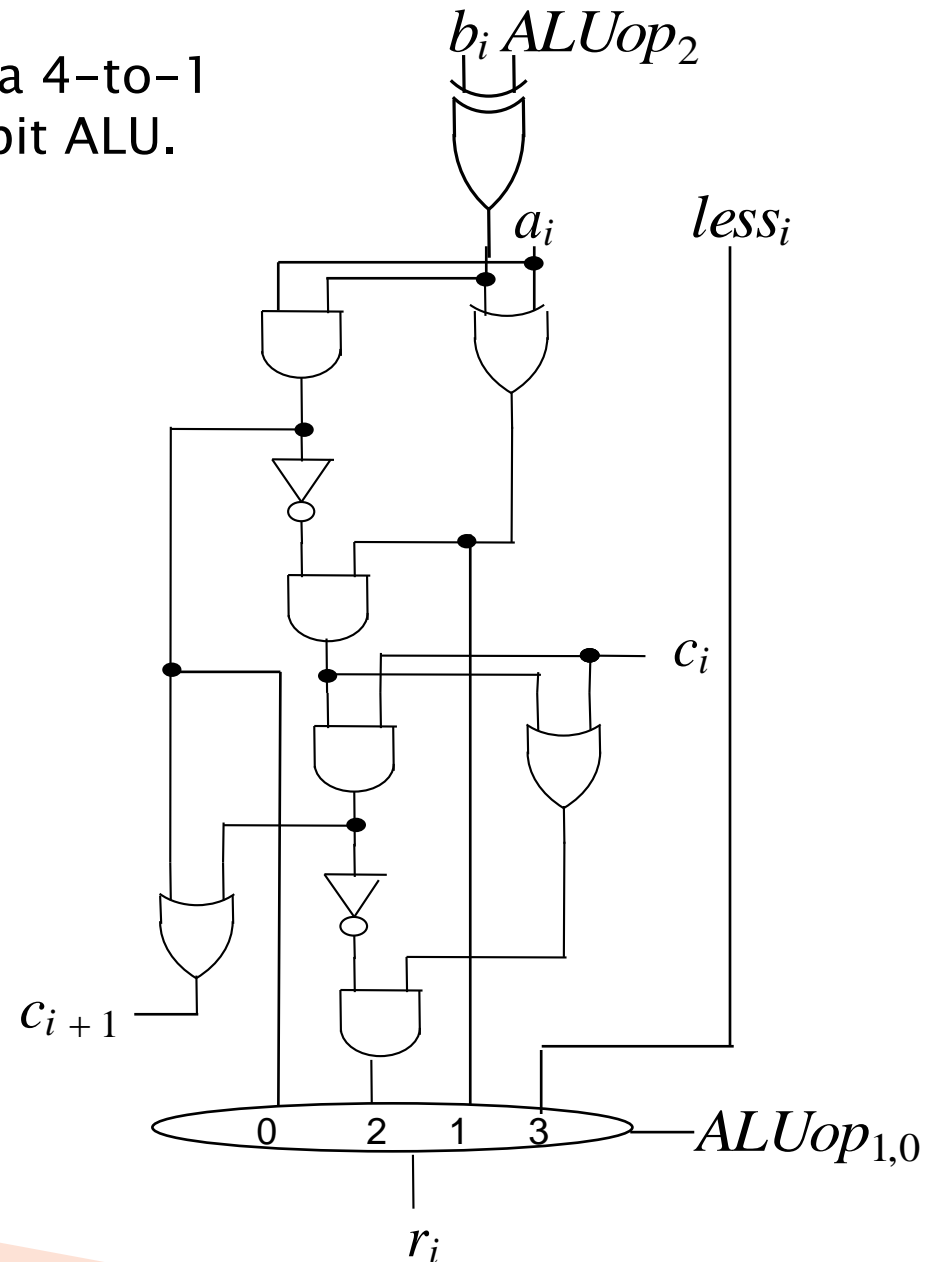


1-bit ALU for MSB

- ▶ The ALU for the MSB must also detect overflow and indicate the sign of the result.


$$V = c_n \otimes c_{n-1}$$

$$set = (A < B)$$

 


Larger ALUs

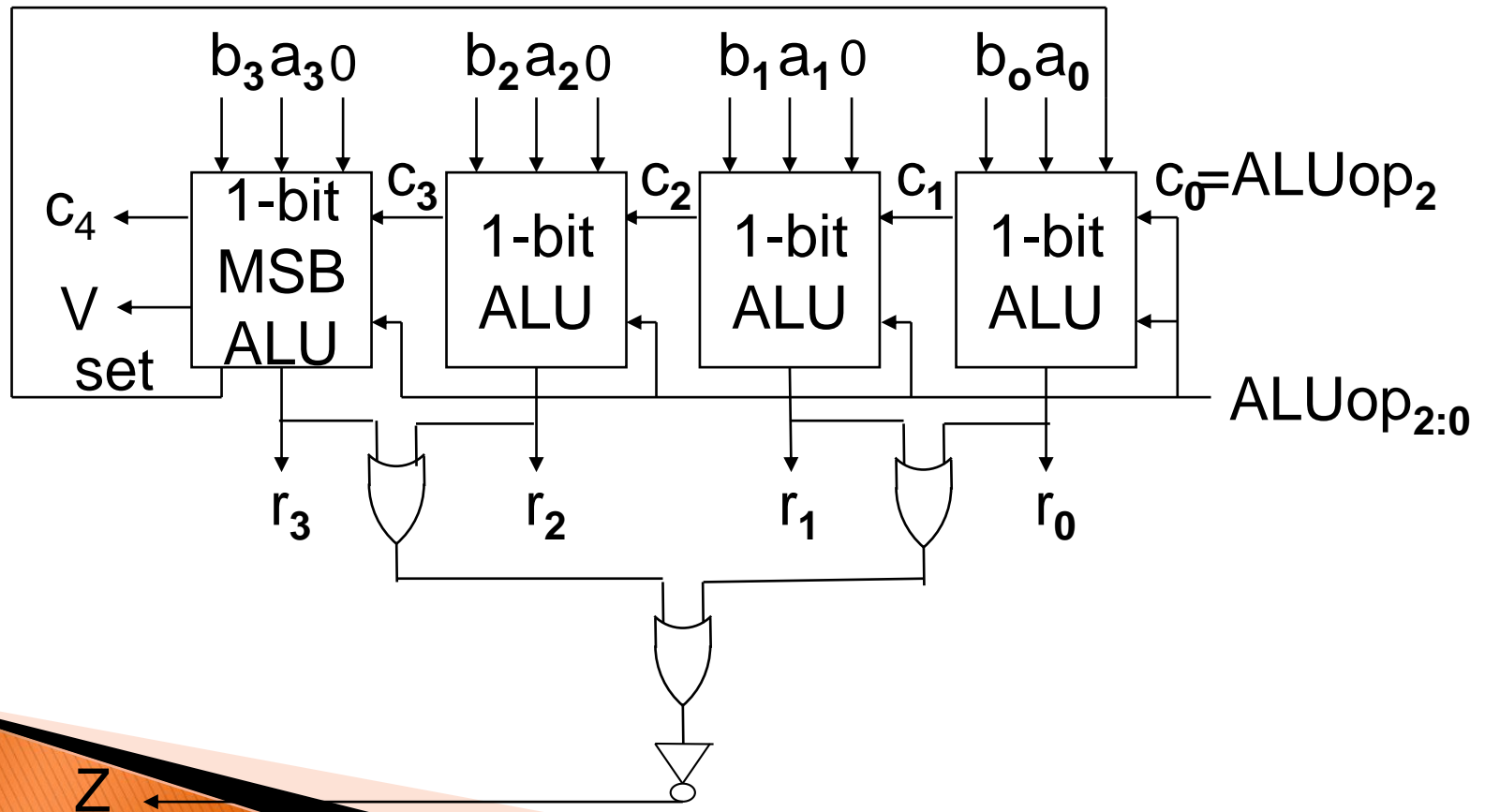- Three 1-bit ALUs, a 1-bit MSB ALU, and a 4-input NOR gate can be concatenated to form a 4-bit ALU.




Gate Counts

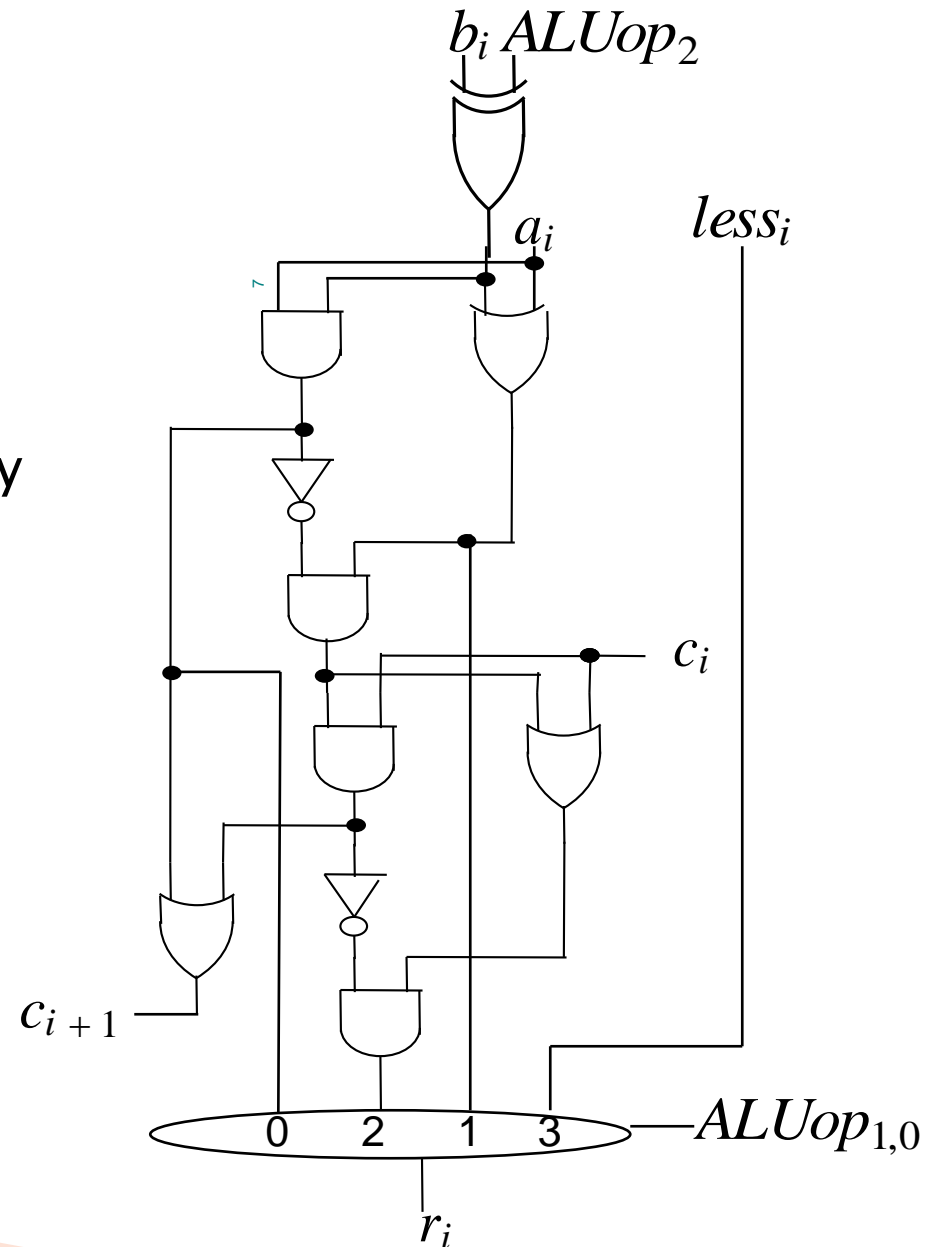- ▶ Assume
 - 4-input mux = 5 gates
 - XOR gate = 3 gates
 - AND/OR gate = 1 gate
 - Inverter = 0.5 gates.
- ▶ How many gates are required by
 - A 1-bit ALU?
 - A 4-bit ALU?
 - A 32-bit ALU?
 - An n-bit ALU?
- ▶ Additional gates needed to compute V and Z




Gate Counts

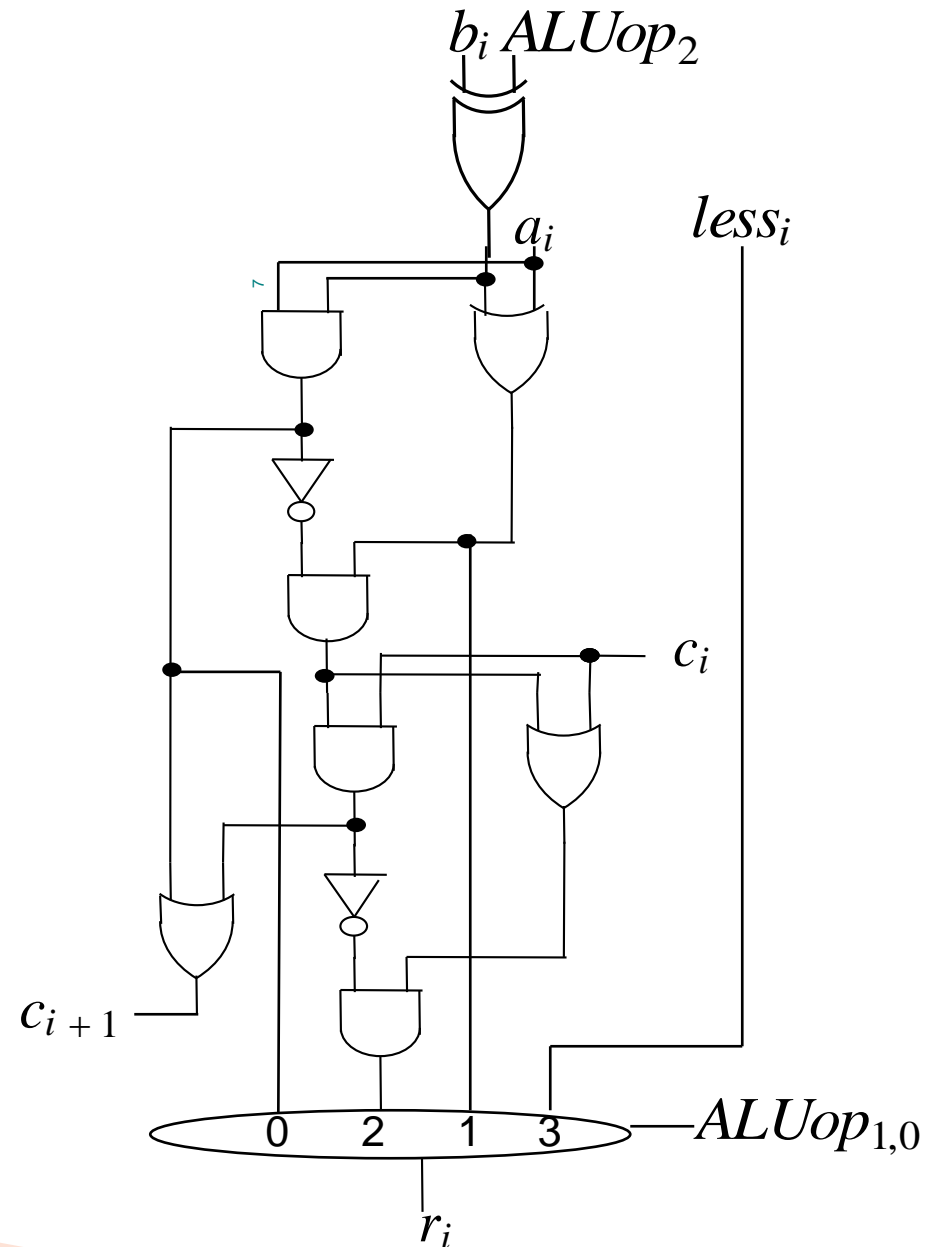- ▶ Assume
 - 4-input mux = 5 gates
 - XOR gate = 3 gates
 - AND/OR gate = 1 gate
 - Inverter = 0.5 gates.
- ▶ How many gates are required by
 - A 1-bit ALU? 16
 - A 4-bit ALU? 16×4
 - A 32-bit ALU? 16×32
 - An n-bit ALU? $16 \times n$
- ▶ $(n-1)$ 2-input OR gates, 1 inverter and 1 XOR gate are needed to compute V and Z for an n-bit ALU




Gate Delays

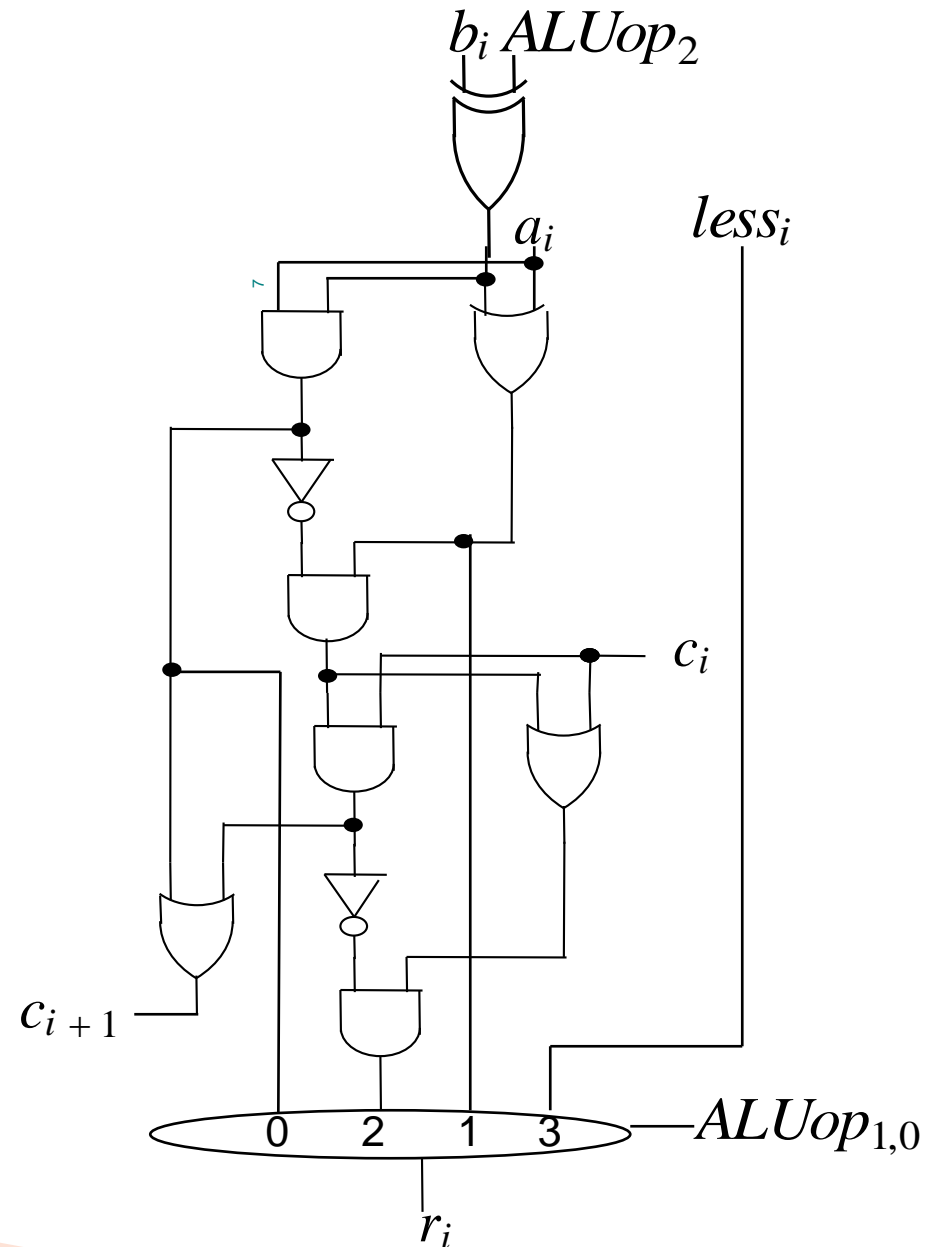- ▶ Assume delays of
 - 4-input mux = $2t$
 - XOR gate = $2t$
 - AND/OR gate = $1t$
 - Inverter = $1t$
- ▶ What is the delay of
 - A 1-bit ALU?
 - A 4-bit ALU?
 - A 32-bit ALU?
 - An n -bit ALU?
- ▶ Additional delay needed to compute Z



Ripple Carry Adder (RCA)

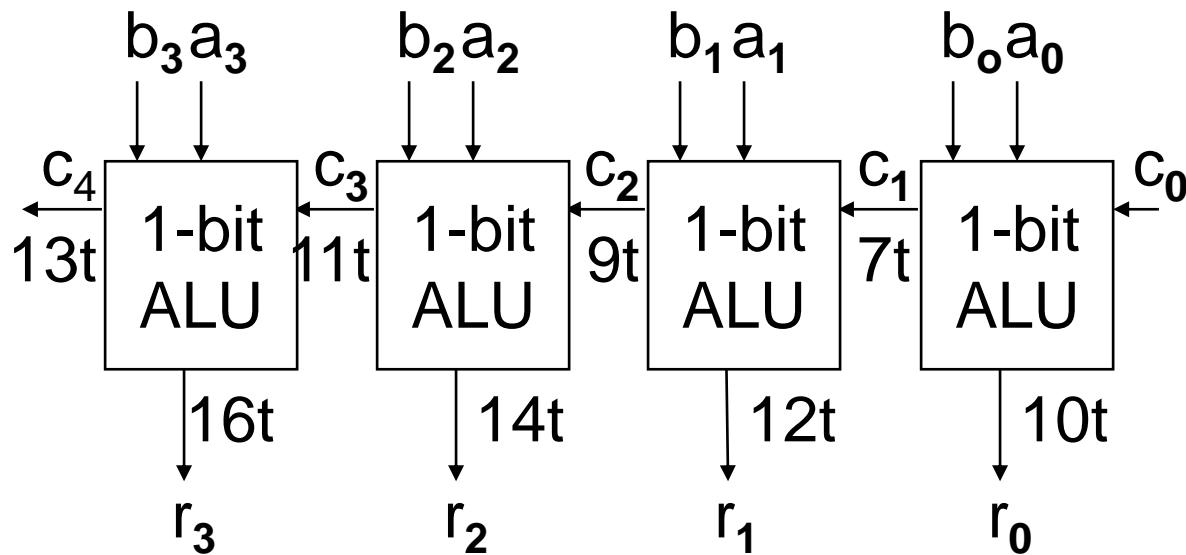
- ▶ With the previous design the carry “rippled” from one 1-bit ALU to the next.



- ▶ These leads to a relatively slow design.
- ▶ Z is ready at 19 t


Gate Delays

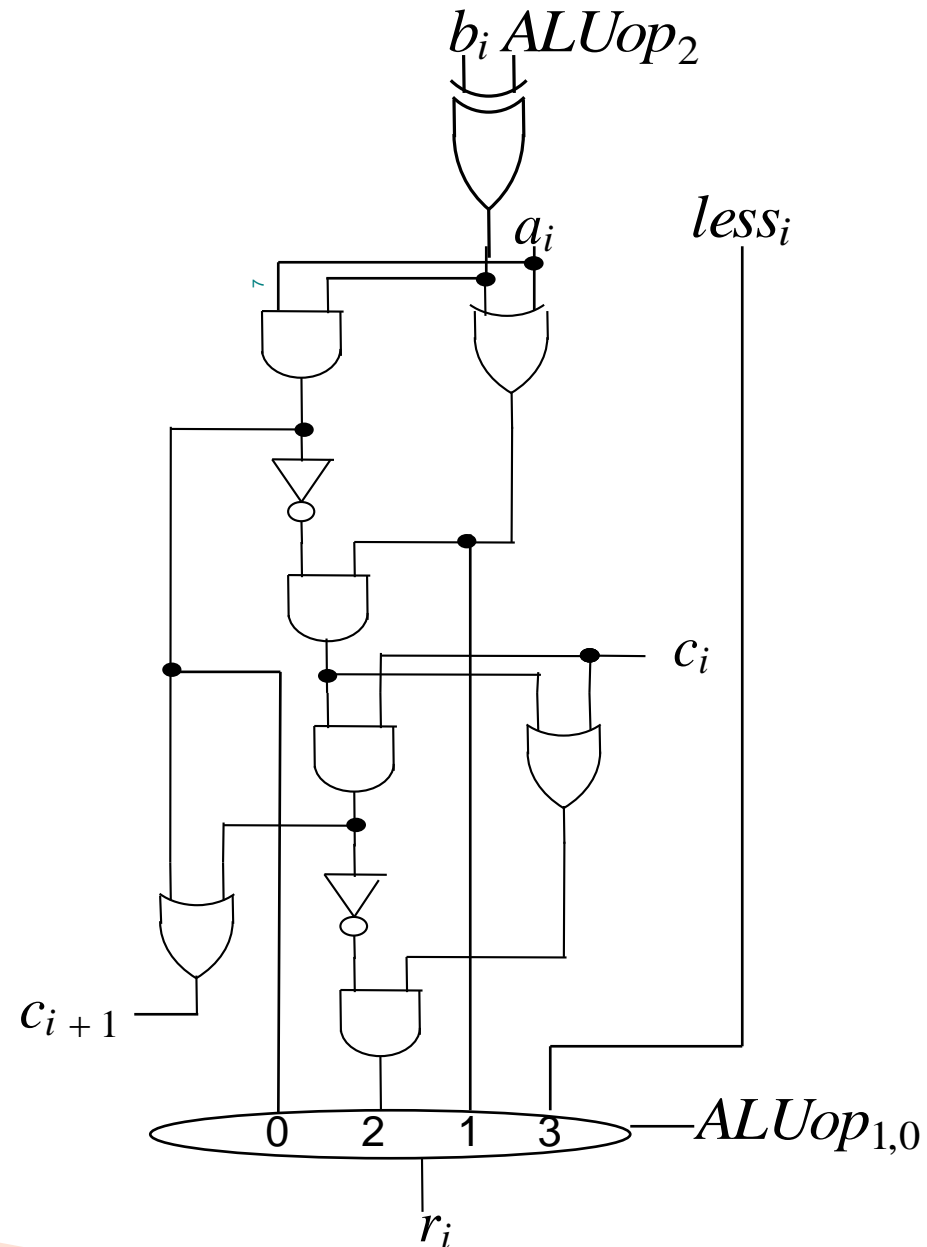- ▶ Assume delays of
 - 4-input mux = $2t$
 - XOR gate = $2t$
 - AND/OR gate = $1t$
 - Inverter = $1t$
- ▶ What is the delay of
 - A 1-bit ALU? $10t$
 - A 4-bit ALU? $16t$
 - A 32-bit ALU? $(2 \times 32 + 8)t = 72t$
 - An n -bit ALU? $(2n + 8)t$
- ▶ $\lceil \log_2(n) \rceil$ levels of 2-input OR gates and 1 inverter are needed to compute Z .



Carry Lookahead Adder (CLA)

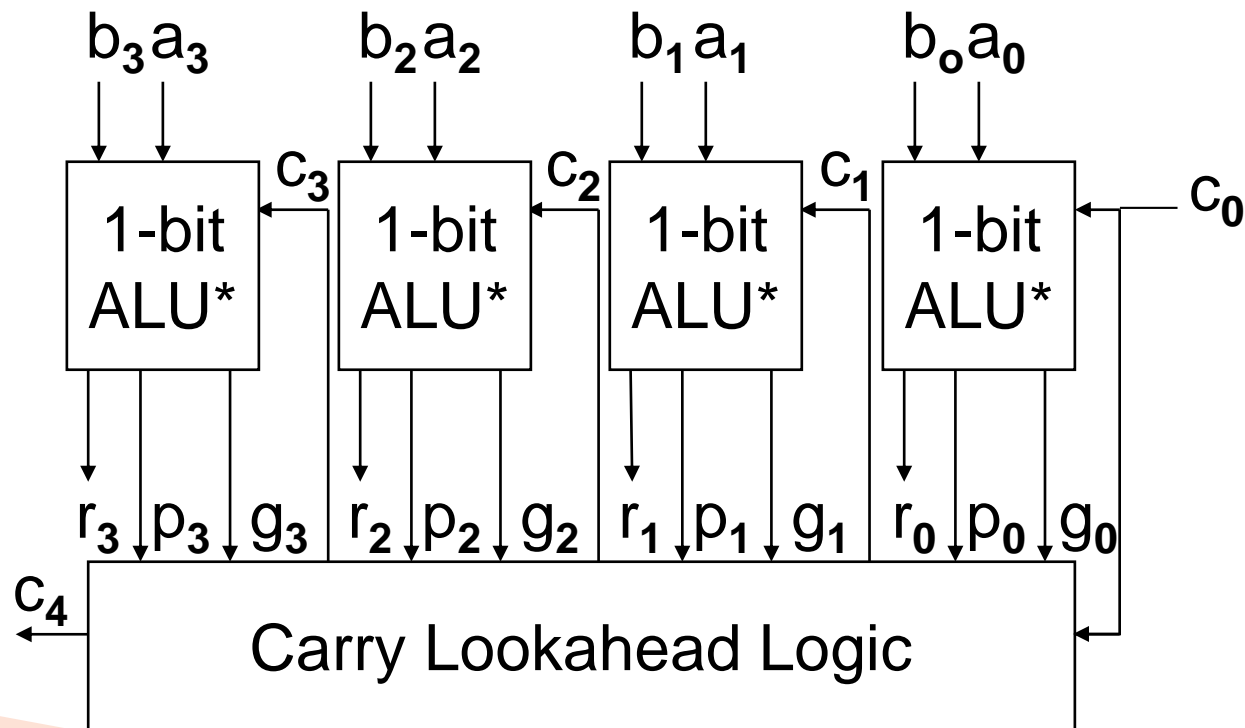- With a CLA, the carries are computed in parallel using carry lookahead logic (CLL).



Carry Logic Equation

- ▶ The carry logic equation is

$$c_{i+1} = a_i b_i + (a_i + b_i) c_i$$

- ▶ We define a propagate signal

$$p_i = a_i + b_i$$

and a generate signal

$$g_i = a_i b_i$$

- ▶ This allows the carry logic equation to be rewritten as

$$c_{i+1} = g_i + p_i c_i$$

Carry Lookahead Logic

7t 9t

- For a 4-bit carry lookahead adder, the carries are computed as

5t $c_1 = g_0 + \underbrace{p_0 c_0}_{4t}$ 1 OR 1 AND

11t (13t)

5t $c_2 = g_1 + \underbrace{p_1 g_0}_{4t} + \underbrace{p_1 p_0 c_0}_{4t}$ 2 AND 1 OR

5t $c_3 = g_2 + \underbrace{p_2 g_1}_{4t} + \underbrace{p_2 p_1 g_0}_{4t} + \underbrace{p_2 p_1 p_0 c_0}_{4t}$ 3 AND 1 OR


(5t) $c_4 = g_3 + \underbrace{p_3 g_2}_{4t} + \underbrace{p_3 p_2 g_1}_{4t} + \underbrace{p_3 p_2 p_1 g_0}_{4t} + \underbrace{p_3 p_2 p_1 p_0 c_0}_{4t}$ 4 AND 1 OR

- How many gates does the 4-bit CLL require, if gates can have unlimited fan-in?
- If each logic level has a delay of only 1t, the CLL has a delay of 2t. => In practice this may not be realistic.

14 additional gates


Modifying the 1-bit ALU

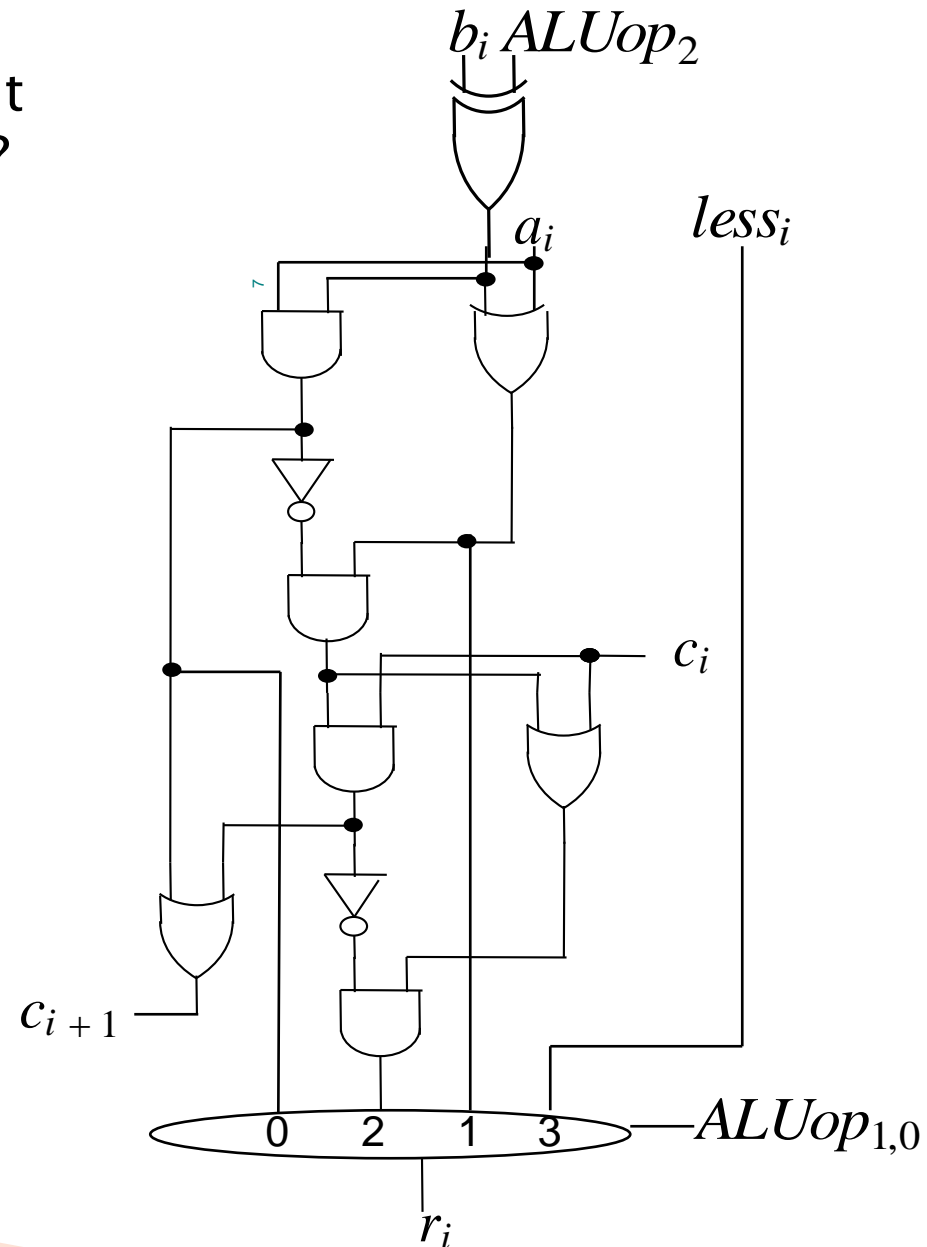- ▶ How would we modify our 1-bit ALU if it is to be used in a CLA?
- ▶ How many gates does the modified 1-bit ALU require?
- ▶ How many gates does a 4-bit CLA require?
- ▶ How many gate delays until p_i and g_i are ready?



4-bit CLA Timing

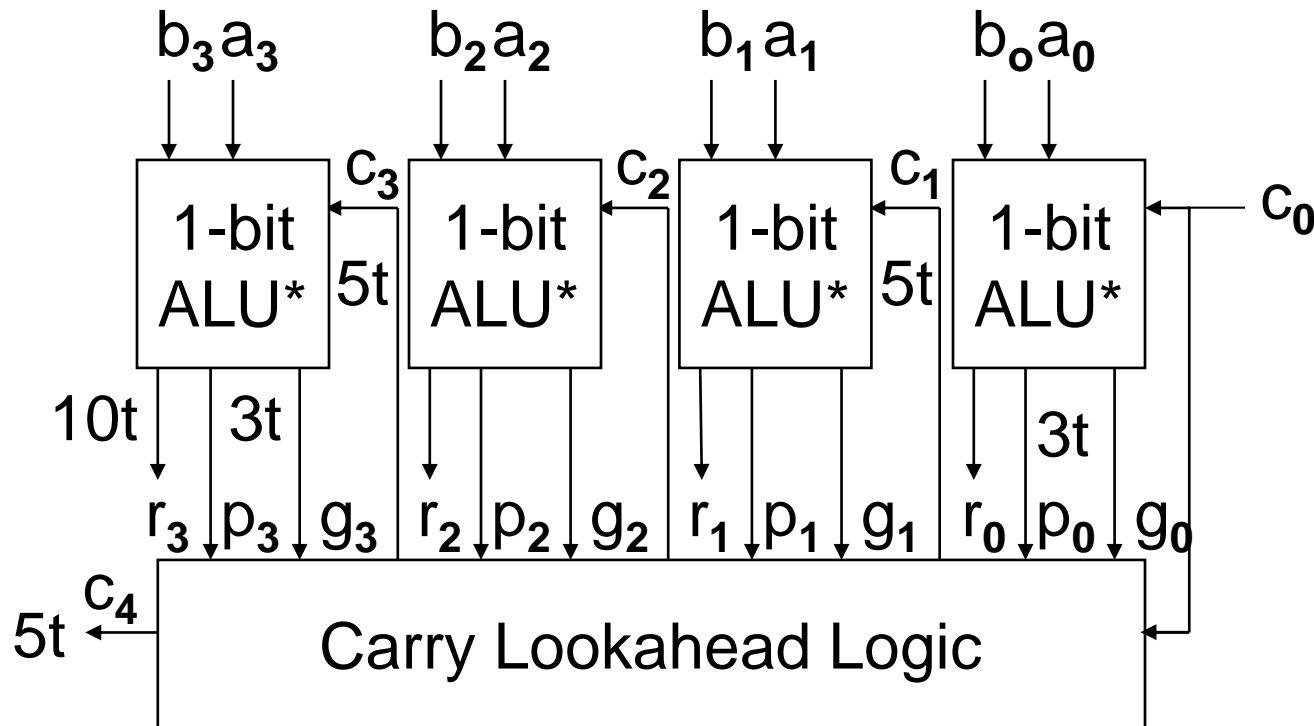
- With a carry lookahead adder, the carries are computed in parallel using carry lookahead logic.



- This design requires $15 \times 4 + 14 = 74$ gates, without computing V or Z

16-bit ALU – Version 1

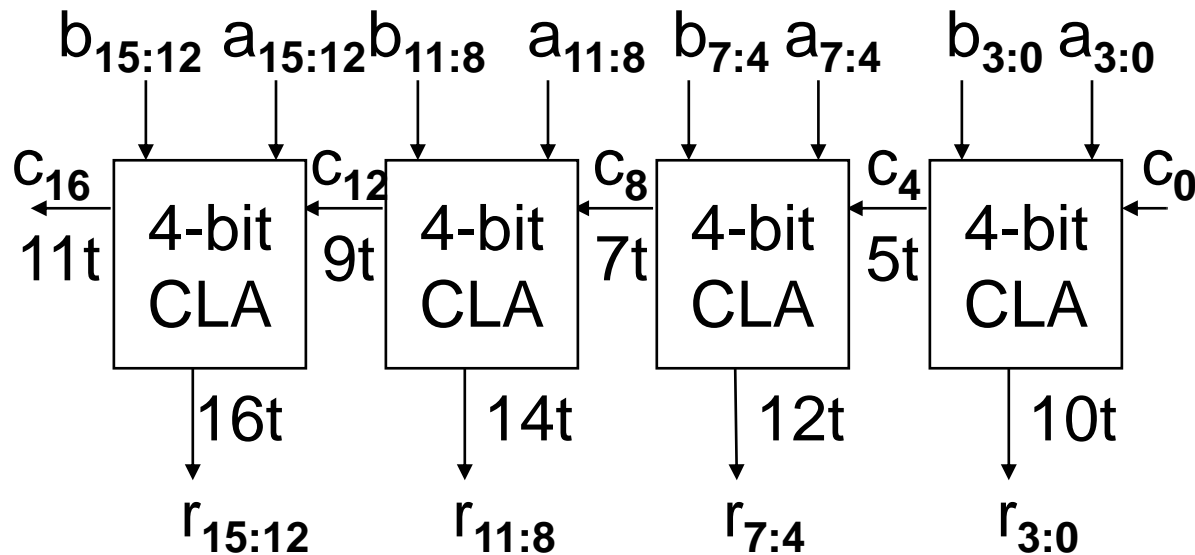
- ▶ A 16-bit ALU could be constructed by concatenating four 4-bit CLAs and letting the carry “ripple” between 4-bit “blocks”.



- ▶ This design requires $74 \times 4 = 296$ gates, without computing V or Z.

16-bit ALU – Version 2

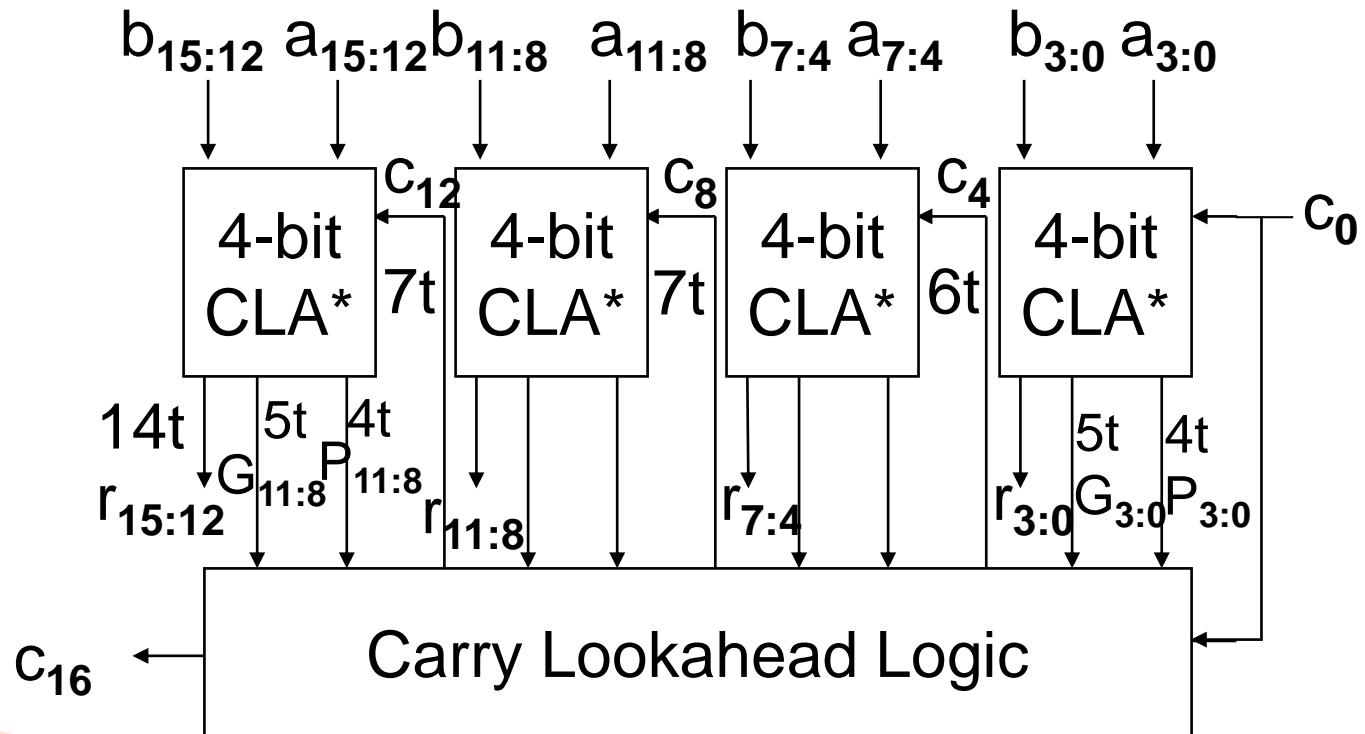- ▶ Another approach is to use a second level of carry lookahead logic.
- ▶ This approach is faster, but requires more gates
 $16 \times 15 + 5 \times 14 = 310$ gates



4-bit CLA*

- ▶ The 4-bit CLA* (Block CLA) is similar to the first 4-bit CLA, except the CLL computes a “block” generate and “block propagate”, instead of a carry out.

- ▶ Thus the computation

$$c_4 = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0 + p_3p_2p_1p_0c_0$$

is replaced by

$$P_{3:0} = p_3p_2p_1p_0$$

$$G_{3:0} = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0$$

- ▶ Note: $c_4 = G_{3:0} + P_{3:0}c_0$
- ▶ This approach limits the maximum fan-in to four, and the carry-lookahead logic still requires 14 gates.

Conclusions

- ▶ An n -bit ALU can be designed by concatenating n 1-bit ALUs.
 - ▶ Carry lookahead logic can be used to improve the speed of the computation.
 - ▶ A variety of design options exist for implementing the ALU.
 - ▶ The best design depends on area, delay, and power requirements, which vary based on the underlying technology.
- 